

Control Design of DC Microgrid Considering CPL Instability

Avanish Dhapare¹ Aditya R. Jadhav¹

¹Department of Electrical Engineering, Indian Institute of Technology (BHU) Varanasi
Mentoring Professor : Dr. Avirup Maulik

April 23, 2024



Table of Contents

- 1 Introduction
- 2 Buck Converter Mathematical Modeling
- 3 Controller Design and Simulation
- 4 Solar Photovoltaic Unit(Non-Dispatchable Unit)
- 5 Simulating the Control Loop
- 6 State Space Modelling and CPL Instability
- 7 Virtual Conductance
- 8 Virtual Capacitance
- 9 Conclusion

DC Micro Grid: Advantages and Challenges

AC Micro Grids are widely used but **DC Micro Grids** are also becoming Popular

Advantages:


- Simpler Controllability due to absence of frequency controlling and phase unbalance.
- Losses like Skin Effect automatically eliminated.

Disadvantages:

- Complicated and Costly Protection System.

Challenges Addressed:

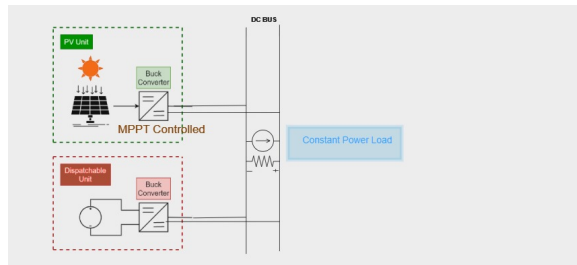- Addressing CPL Instability
- Lack of Inertia leading to high ROCOV



Dispatchable Unit(Grid Forming Unit):

- Output voltage is tracked keeping the *DC Bus Link Voltage constant*


PV Unit:

- Idea is to track Input Voltage To Maximum Power Point Voltage by Implementing MPPT Algorithms

Table of Contents

- 1 Introduction
- 2 Buck Converter Mathematical Modeling**
- 3 Controller Design and Simulation
- 4 Solar Photovoltaic Unit(Non-Dispatchable Unit)
- 5 Simulating the Control Loop
- 6 State Space Modelling and CPL Instability
- 7 Virtual Conductance
- 8 Virtual Capacitance
- 9 Conclusion

Buck Converter Topology

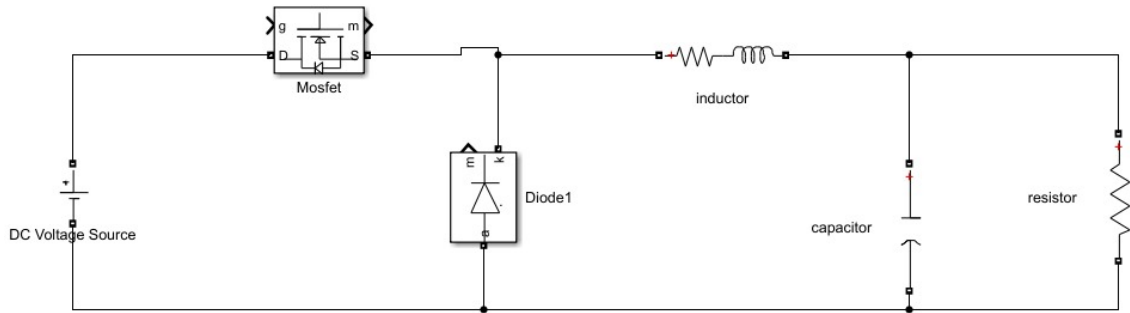


ON mode OFF Mode
Analysis

State Space Averaging

Linearized Model

Small Signal Analysis


Mode 1

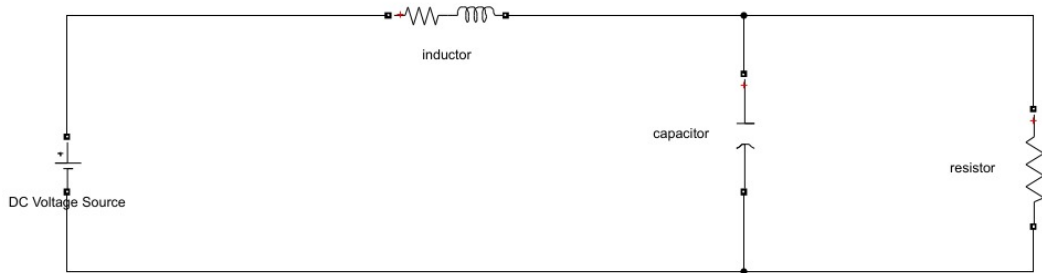

$$V_i = L \frac{di}{dt} + i r_s + V \quad (1)$$

$$i = C \frac{dV}{dt} + \frac{V}{R} \quad (2)$$

Mode 2

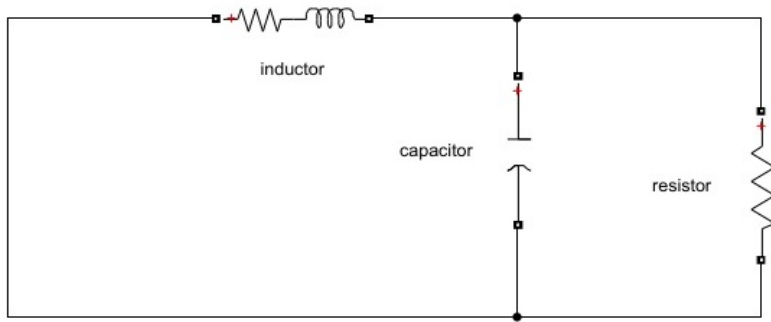

$$0 = L \frac{dV}{dt} + ir_s + V \quad (3)$$

$$i = C \frac{dV}{dt} + \frac{dV}{dt} \quad (4)$$

State Space Averaging

$$DV_i = L \frac{di}{dt} + iR_s + V \quad (5)$$

$$i = C \frac{dV}{dt} + \frac{V}{R} \quad (6)$$

Linearizing the Model Under Steady State With **Small Ripple Approximation**

Linearizing

$$D = D_o + \hat{d}$$


$$V = V_o + \hat{v}$$

$$I = I_o + \hat{i}$$

Small Ripple Approximation

$$D_o V_i = I_o r_s + V_o \quad (7)$$

$$I_o = \frac{V_o}{R} \quad (8)$$

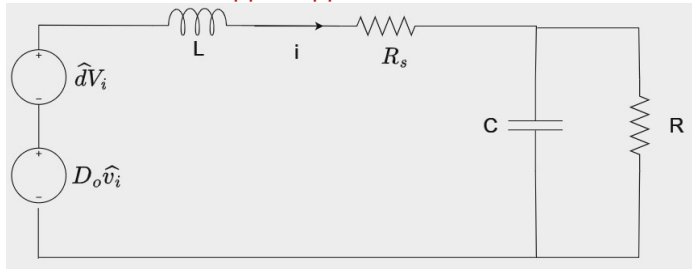

$$D_o \hat{v}_i + \hat{d}V_i = L \frac{d\hat{i}}{dt} + r_s \hat{i} + \hat{v}$$

$$\hat{i} = C \frac{d\hat{v}}{dt} + \frac{\hat{v}}{R}$$

Table of Contents

- 1 Introduction
- 2 Buck Converter Mathematical Modeling
- 3 Controller Design and Simulation**
- 4 Solar Photovoltaic Unit(Non-Dispatchable Unit)
- 5 Simulating the Control Loop
- 6 State Space Modelling and CPL Instability
- 7 Virtual Conductance
- 8 Virtual Capacitance
- 9 Conclusion

Voltage Controller Design

From Small Signal Model:

$$\hat{i} = C \frac{d\hat{v}}{dt} + \frac{d\hat{v}}{dt}$$

$$I(s) = CsV(s) + \frac{V(s)}{R}$$

$$\frac{V(s)}{I(s)} = \frac{R}{1 + RCs}$$

Current Controller Design

From Small Signal Model:

$$\hat{d}V_i - \hat{v} = L \frac{d\hat{i}}{dt} + r_s \hat{i} = u$$


$$U(s) = sLI(s) + R_s I(s)$$

$$\frac{I(s)}{U(s)} = \frac{1}{R_s + sL}$$

PI Parameter Tuning

Current Controller
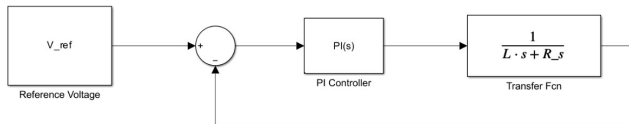
$$G(s) = \frac{sK_p + K_i}{s(R_s + sL)} = \frac{K_i(1 + \frac{sK_p}{K_i})}{sR(1 + \frac{sL}{R})}$$



By Pole Zero Cancellation

$$G(s) = \frac{K_i}{sR} = \frac{1}{s\tau}$$

Where

$$\tau = \frac{R_s}{K_i} \text{ and } \omega_o = \frac{1}{\tau} = \frac{2\pi f_s}{20}$$

Thumb Rule

Bandwidth of Inner Loop Should be 10 to 20 Times Lower than that of Switching Frequency


$$K_i = \frac{R_s}{\tau} = \frac{2\pi f_s R_s}{20}$$

$$K_p = \frac{2\pi f_s L}{20}$$

PI Parameter Tuning

Voltage Controller
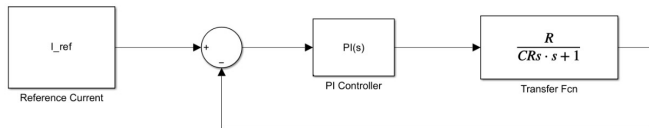
$$G(s) = \frac{(sK_p + K_i)R}{s(1 + sCR)} = \frac{RK_i(1 + \frac{sK_p}{K_i})}{s(1 + sCR)}$$



By Pole Zero Cancellation

$$G(s) = \frac{K_i R}{s} = \frac{1}{s\tau}$$

Where

$$\tau = \frac{1}{K_i R} \text{ and } \omega_o = \frac{1}{\tau} = \frac{2\pi f_s}{100}$$


Thumb Rule

Outer Loop Should be 10 Times Slower Than The Inner Loop

$$K_i = \frac{1}{R\tau} = \frac{2\pi f_s}{100R}$$

$$K_p = \frac{2\pi f_s C}{100}$$

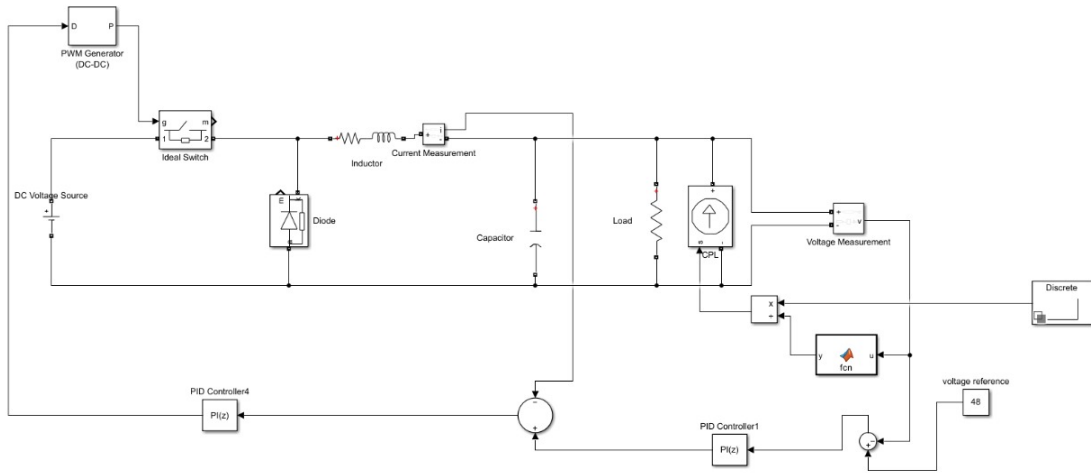Implementation of Control Loop in Buck Converter



Simulation Results


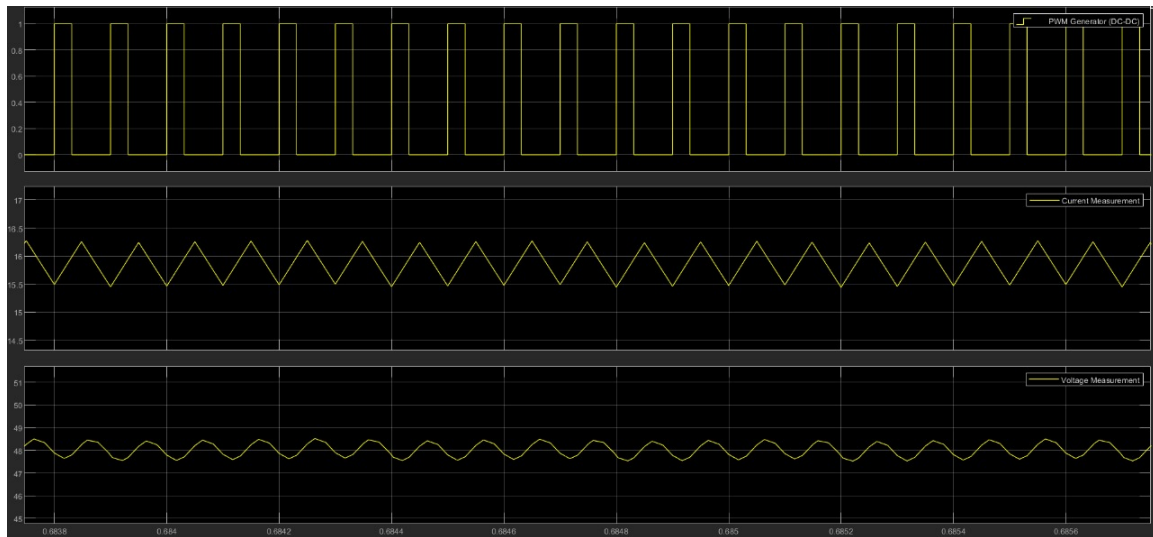


Table of Contents

- 1 Introduction
- 2 Buck Converter Mathematical Modeling
- 3 Controller Design and Simulation
- 4 Solar Photovoltaic Unit(Non-Dispatchable Unit)**
- 5 Simulating the Control Loop
- 6 State Space Modelling and CPL Instability
- 7 Virtual Conductance
- 8 Virtual Capacitance
- 9 Conclusion

Non Dispatchable Unit

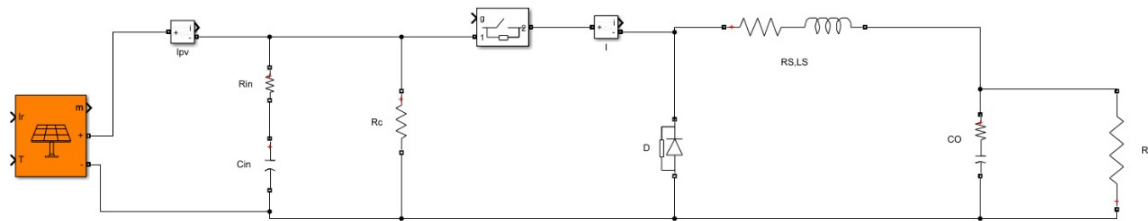

ON mode OFF Mode
Analysis

State Space Averaging

Linearized Model

Small Signal Analysis

State Space Averaging

State Space Average Model is Given by:

$$i_{pv} = C_i \frac{dV_i}{dt} + Di + \frac{V_i}{R_c}$$

$$DV_i = L \frac{di}{dt} + R_s i + V_o$$

Small Signal Model is Given as:


$$\hat{i}_{pv} = C_i \frac{d\hat{V}_i}{dt} + \hat{d}i_o + D_o \hat{i}$$

$$D_o \hat{V}_i + \hat{d}V_{io} = L \frac{d\hat{i}}{dt} + R_s \hat{i}$$

Table of Contents

- 1 Introduction
- 2 Buck Converter Mathematical Modeling
- 3 Controller Design and Simulation
- 4 Solar Photovoltaic Unit(Non-Dispatchable Unit)
- 5 Simulating the Control Loop**
- 6 State Space Modelling and CPL Instability
- 7 Virtual Conductance
- 8 Virtual Capacitance
- 9 Conclusion


Simulating the Control Loop

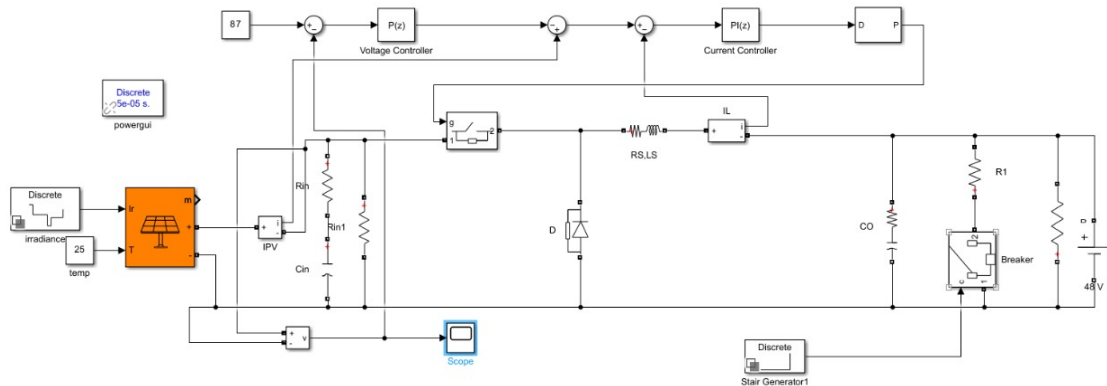

NOTE

A DC source is used to maintain output voltage at 48. Practically however the DC Bus Link Voltage is maintained by the Dispatchable Unit(Grid Forming Unit)

Simulation Results

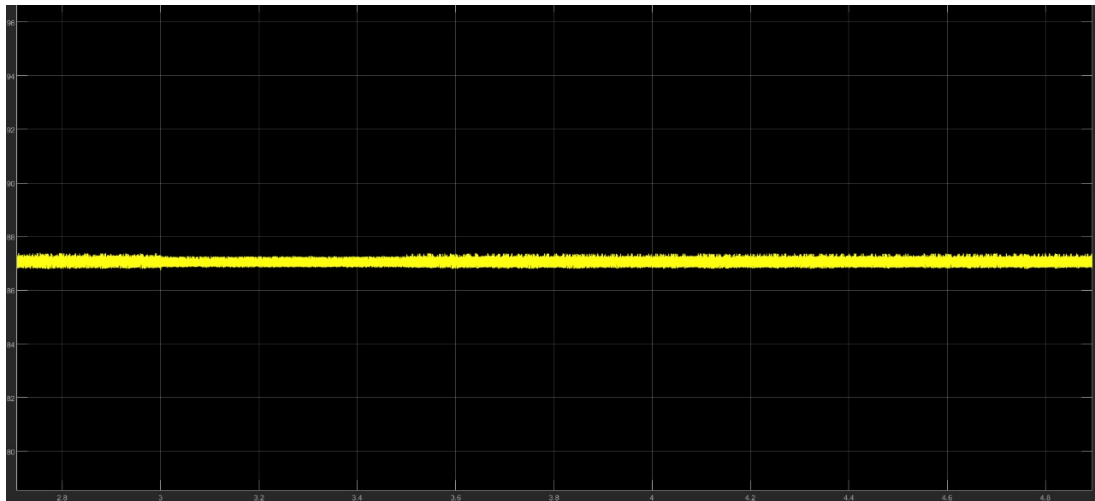

Maximum Power Point Voltage = 87 was Tracked

Table of Contents

- 1 Introduction
- 2 Buck Converter Mathematical Modeling
- 3 Controller Design and Simulation
- 4 Solar Photovoltaic Unit(Non-Dispatchable Unit)
- 5 Simulating the Control Loop
- 6 State Space Modelling and CPL Instability**
- 7 Virtual Conductance
- 8 Virtual Capacitance
- 9 Conclusion

State Space Model

State Space Model is Given By:

$$\frac{dx}{dt} = Ax + B_1W + B_2U$$


x : state space variables

W : disturbances

U : input *State Space Model for*

Dispatchable + Non-Dispatchable Unit
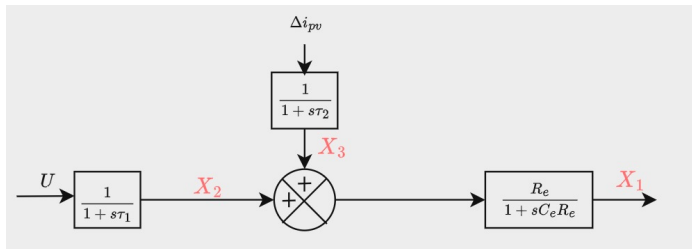
$$A = \begin{bmatrix} \frac{-1}{R_e C_e} & \frac{1}{C_e} & \frac{1}{C_e} \\ 0 & \frac{-1}{\tau_1} & 0 \\ 0 & 0 & \frac{-1}{\tau_2} \end{bmatrix}$$



R_e = Equivalent Resistance

C_e = Equivalent Capacitance

τ_1 = Time Constant of Current Controller of Dispatchable Unit

τ_2 = Time Constant of Current Controller of Solar Unit

Small Signal Model

For constant Power Load:


$$P = VI$$

$$P_o + \Delta p = (V_o + \Delta v)(I_o + \Delta i)$$

$$\Delta p = \Delta v I_o + V_o \Delta i$$

$$\Delta i = \frac{\Delta p}{V_o} - \frac{\Delta v}{\left(\frac{V_o}{I_o}\right)}$$
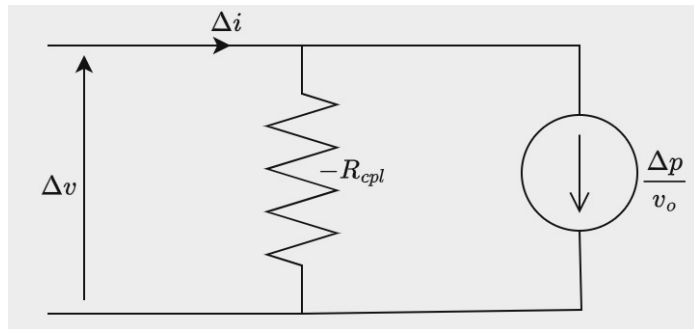
$$\Delta i = \frac{\Delta p}{V_o} - \frac{\Delta v}{R_{cpl}}$$



- CPL introduces a **negative resistance** in the small signal model.
- The negative resistance causes **instability in the physical system**.

Eigenvalue Calculation For Varying CPL

- Eigenvalues of Matrix A for 4 different values of CPL are tabulated

Eigenvalues	R = 10	R = 5	R = -5	R = -10
λ_1	-475.8	-951.6	951.6	475.8
λ_2	-314.16	-314.16	-314.16	-314.16
λ_3	-314.16	-314.16	-314.16	-314.16

$\lambda_i = i^{th} \text{eigenvalue}$

- All eigenvalues in left half plane for positive CPL
- Some eigenvalues in left half plane for negative CPL

	λ_1	λ_2	λ_3
X_1	1	0	0
X_2	0	1	0
X_3	0	0	1

Table: Participation Factor Analysis

Table of Contents



- 1 Introduction
- 2 Buck Converter Mathematical Modeling
- 3 Controller Design and Simulation
- 4 Solar Photovoltaic Unit(Non-Dispatchable Unit)
- 5 Simulating the Control Loop
- 6 State Space Modelling and CPL Instability
- 7 Virtual Conductance**
- 8 Virtual Capacitance
- 9 Conclusion

Mitigating CPL Instability Using Virtual Conductance

$$i = C \frac{dv}{dt} + G_v v - G v$$

- Virtual Conductance neutralizes effect of negative CPL
- Magnitude of G_v should be *greater than maximum magnitude of negative CPL*
- Called virtual because it is not a physical impedance but **implemented in control loop**
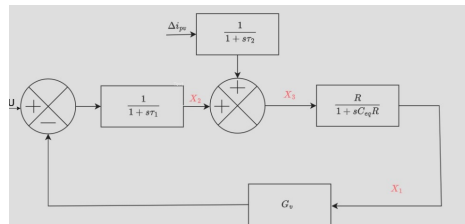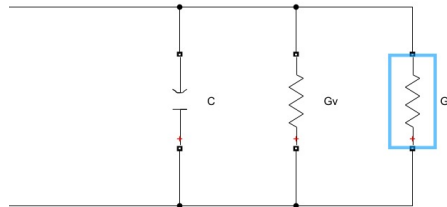
$$A = \begin{bmatrix} \frac{-1}{R_e C_e} & \frac{1}{C_e} & \frac{1}{C_e} \\ \frac{G_v}{\tau_1} & \frac{-1}{\tau_1} & 0 \\ 0 & 0 & \frac{-1}{\tau_2} \end{bmatrix}$$




Eigenvalue Tabulation(with Virtual Conductance)

Eigenvalues	R = 10	R = 5
λ_1	-0.0181 + 1.2225i	-0.0205 + 1.2226i
λ_2	-0.0181 - 1.2225i	-0.0205 - 1.2226i
λ_3	-0.0314	-0.0314

Eigenvalues	R = -5	R = -10
λ_1	-0.0109 + 1.2224i	-0.0133 + 1.2225i
λ_2	-0.0109 - 1.2224i	-0.0133 - 1.2225i
λ_3	-3.1416	-0.0314

$\lambda_i = i^{th}$ eigenvalue
All Eigenvalues Lie
in the Left Half
Plane

Simulation Results

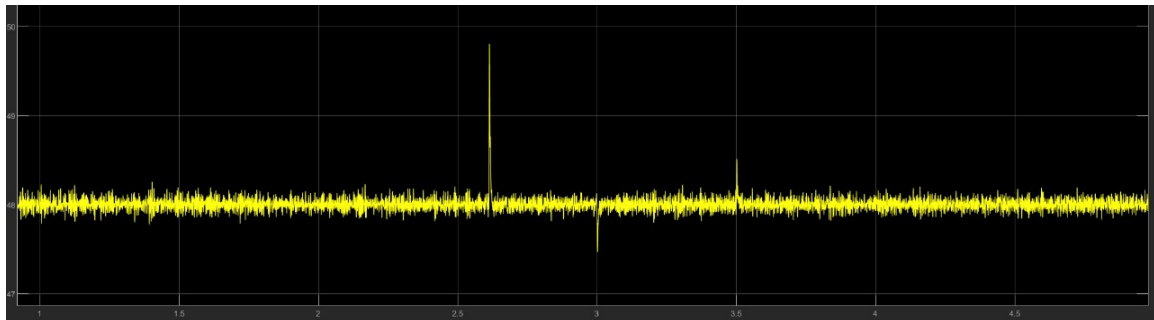

2nd Challenge

Overshoots undershoots seen due to *changes in Irradiance*

Table of Contents


- 1 Introduction
- 2 Buck Converter Mathematical Modeling
- 3 Controller Design and Simulation
- 4 Solar Photovoltaic Unit(Non-Dispatchable Unit)
- 5 Simulating the Control Loop
- 6 State Space Modelling and CPL Instability
- 7 Virtual Conductance
- 8 Virtual Capacitance**
- 9 Conclusion

Virtual Capacitance


$$i = C \frac{dv}{dt} + \frac{v}{R} + C_v \frac{dv}{dt}$$

$$i - C_v \frac{dv}{dt} = C \frac{dv}{dt} + \frac{v}{R}$$


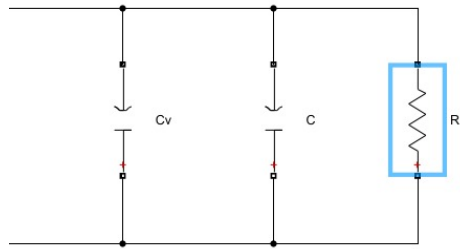
- Virtual Capacitance helps in **reduction of ROCOV**
- Positive voltage slope decreases current and negative slope increases it
- Physical implementation of capacitor is *expensive* so it is **implemented in control loop**



Simulation Results

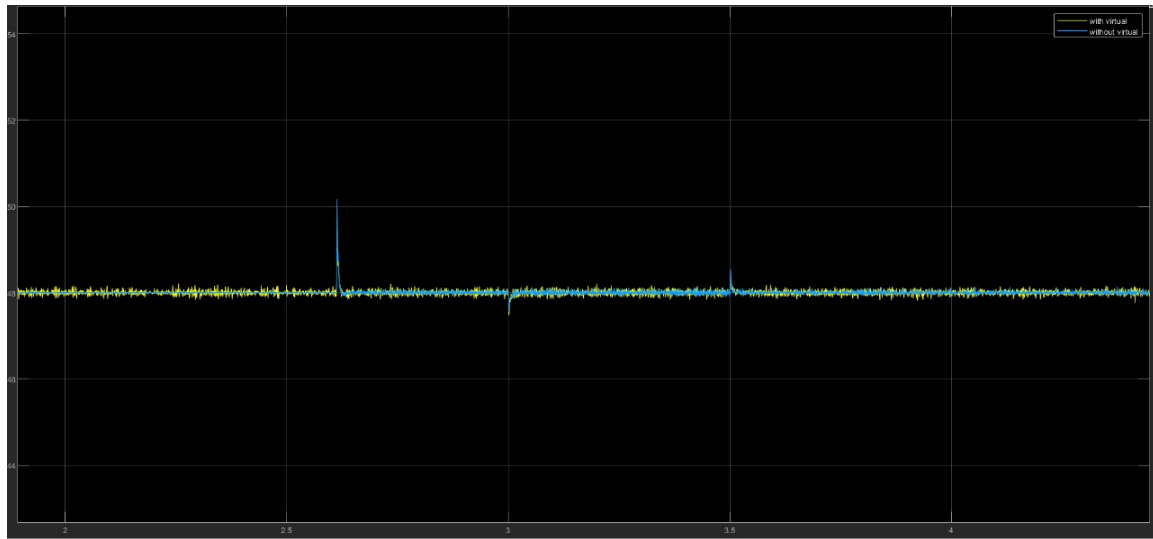

Simulation Results

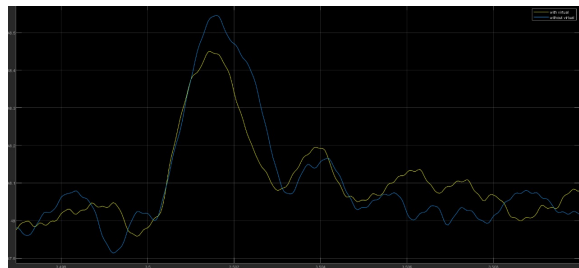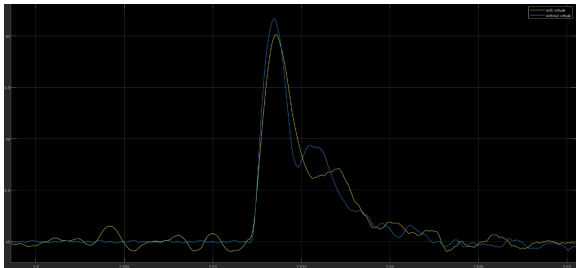

Magnitudes of overshoots is more for system without virtual capacitance

Table of Contents

- 1 Introduction
- 2 Buck Converter Mathematical Modeling
- 3 Controller Design and Simulation
- 4 Solar Photovoltaic Unit(Non-Dispatchable Unit)
- 5 Simulating the Control Loop
- 6 State Space Modelling and CPL Instability
- 7 Virtual Conductance
- 8 Virtual Capacitance
- 9 Conclusion**

Conclusion

- CPL instability due to introduction of negative resistance in the small signal model is addressed by **Implementing Virtual Conductance in the Control Loop**
- Lack of Inertia Causing high ROCOV mitigated by **Implementing Virtual Capacitance**.

Future Works

- Designing of Bidirectional Converter to handle Situations of **Overgeneration of Power**
- Real Time Implementation using **DSP Signals and RTDS Integration**